

Ahsanullah University of Science and Technology

Department of Computer Science and Engineering


CSE 2210: Digital Electronics and Pulse Techniques Lab

Group: B1

Experiment # 3

Name of the experiment: Study of a TTL NAND gate with totem-pole output.

Circuit Diagram:

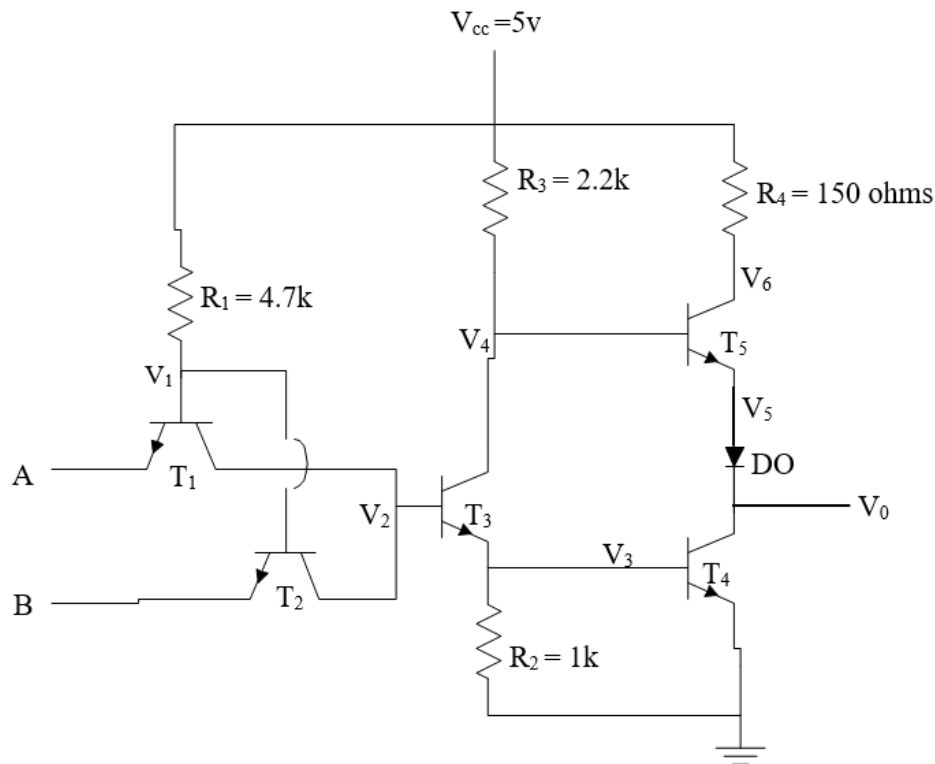

Procedure:

1. Measure the V_0 , V_1 , V_2 , V_3 , V_4 , V_5 & V_6 for all possible input combinations.
2. Calculate noise margins.

Questions:

1. Analyze the operation of TTL NAND gate with the experimental data.
2. What are the differences of transistors T_1 & T_2 with that of a multi-emitter transistor? [Hint: Millman Sec 4-7,5-11]
3. What is totem-pole stage? Why it is used in place of passive pull-up resistor? [Hint: Millman Sec 5-12]
4. What is the function of T_3 ? [Hint: Millman Sec 5-12]
5. Why resistor R_4 is used? [Hint: Millman Sec 5-12]
6. Why diode D_0 is used in the circuit? Can it be placed elsewhere? [Hint: Millman Sec 5-12]
7. Why two totem pole gates cannot be wire ANDed? [Hint: Millman pg. 151]
8. What are the features and advantages of TTL gates? [Hint: Millman Sec 5-15]

Report:

1. Objective.
2. Circuit diagram.
3. Answer to the questions.
4. Experimental data.
5. Calculations.
6. Discuss the findings.

This is a theoretical explanation. Your NM(0) and NM(1) will change according to the measurement you have taken. Do not copy-paste these values directly to your lab report.

NM(0):

Negative Spike:

For all inputs high, the output should be low. So, a negative spike will change the output to high. For the given circuit, if T_3 and T_4 will have to stop conducting to change the output to high.

We consider the case of the negative spike. We know that a diode will start conducting at 0.6 volts. emitter-base junction of T_1 and T_2 can be considered as a diode. So it will start conducting when it gets at least 0.6 volts.

When all input 1, Suppose $V_2 + V_3 = 1.44 + 0.728 = 2.168$ V. So, $NM(0) = - (5 - 2.168) = -2.832$ V

NM(1):

Positive Spike:

If only one input is at $V(1)$, and the other is at $V(0)$, then if $V(0)$ tends to increase we need only $0.5 + 0.5 = 1.0$ volt at T_3 's base to make the path along T_3 - T_4 to conduct. Suppose, $V_2 = 0.025$ V

$$NM(1) = 1 - 0.025 = 0.975 \text{ V}$$